

LED CHASER



Session: 2022 – 2026

Submitted by:

Shahbaz Ali	2022-CS-27
M. Nouman	2022-CS-49
Bisma Shakeel	2022-CS-50
Abdul Saboor	2022-CS-10

Submitted to:

Ms. Aroosh Fatima

Department of Computer Science

University of Engineering and Technology
Lahore Pakistan

LED Chaser

Introduction:

The LED Chaser project aims to design and implement a simple yet visually appealing circuit that creates a chasing effect using a sequence of LEDs. This report provides an overview of the project, including its objectives, the components used, the circuit design, and the key findings.

Objectives:

The primary objectives of the project are as follows:

1. Demonstrate the operation and utilization of the 4017 decoder: The project seeks to showcase the functionality of the 4017 decoder as a key component in creating sequential LED lighting effects. It aims to illustrate how the decoder can divide the clock frequency and produce sequential outputs to control the LEDs.
2. Showcase the functionality of the NE555 timer: The project aims to highlight the role of the NE555 timer in generating clock pulses, which serve as the timing mechanism for the LED chaser circuit. It aims to demonstrate how adjusting the clock frequency affects the speed at which the LEDs light up in a sequential pattern.
3. Illustrate the integration of various electronic components: The project seeks to provide a practical example of how different electronic components, such as capacitors, resistors, and potentiometers, can be interconnected to create a functional circuit. It aims to showcase the correct wiring and connection of these components for optimal circuit performance.
4. Create an engaging and visually appealing LED chasing effect: The primary objective of the LED Chaser project is to generate an impressive visual effect by controlling the illumination of multiple LEDs in a sequential pattern. The project aims to design a circuit that

produces an aesthetically pleasing LED chaser display with adjustable speed, allowing for customization and versatility.

5. Enhance understanding of digital logic design principles: By working on the LED chaser project, the objective is to provide individuals with a hands-on experience in digital logic design. It aims to improve knowledge and comprehension of concepts such as clock frequency, sequential logic, and the interaction between electronic components in a practical circuit.


Description:

The LED Chaser project involves the design and implementation of a circuit that creates an engaging LED chasing effect using a sequence of LEDs. The project utilizes several electronic components to achieve the desired visual effect and serves as an educational tool to demonstrate digital logic design principles. To allow for customization and versatility, the project incorporates a POT-HG potentiometer. By adjusting the potentiometer, the clock frequency can be modified, thus altering the speed at which the LEDs light up and creating different chasing effects.

Gate Used:

- 4017 Decoder
- Capacitors (10uF)
- NE555 Timer
- POT-HG (47K Potentiometer)
- Resistors (100 ohm and 2.7K)
- 9V Battery
- LEDs (10 pieces)

Circuit Diagram:

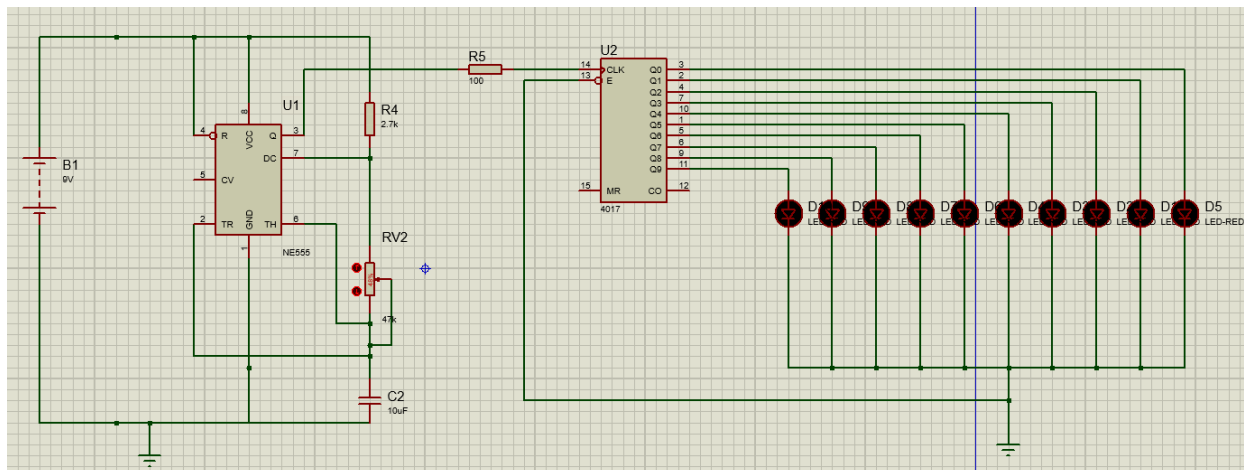

Methodology:

The project followed a systematic approach to achieve its objectives:

1. **Gathering Components:** Begin by collecting all the necessary components required for the LED Chaser project, including the 4017 decoder, capacitors, NE555 timer, POT-HG potentiometer, resistors, 9V battery, and LEDs.
2. **Circuit Design:** Create a circuit diagram or schematic that illustrates the connections and arrangement of the components. Follow the datasheets or reference materials for each component to ensure correct pin configurations and proper wiring.
3. **Component Placement:** Assemble the circuit on a breadboard or PCB (Printed Circuit Board) according to the circuit diagram. Place the components in their designated positions, making sure to connect the appropriate pins and terminals as per the circuit design.
4. **Power Supply:** Connect the 9V battery or power source to the circuit, ensuring proper polarity and voltage requirements are met.

5. **LED Connection:** Connect the LEDs in a sequential manner, forming a pattern that will produce the desired chasing effect. Make sure to connect the anode (longer lead) of each LED to the output pin of the 4017 decoder and the cathode (shorter lead) to the common ground.
6. **Clock Generation:** Connect the NE555 timer to generate clock pulses. Set the timing components (resistors and capacitors) according to the desired clock frequency. The POT-HG potentiometer can be used to adjust the clock frequency and control the speed of the LED chasing effect.
7. **Testing and Troubleshooting:** Power on the circuit and observe the LED chaser effect. Verify that the LEDs light up in a sequential pattern according to the clock pulses. If any issues arise, such as incorrect sequencing or non-functional LEDs, check the connections, component values, and power supply to identify and rectify any potential errors.
8. **Fine-tuning and Customization:** Experiment with different clock frequencies by adjusting the POT-HG potentiometer. Observe how the speed of the LED chasing effect changes, and make adjustments to achieve the desired visual pattern and effect.

Findings:

The project findings can be summarized as follows:

- 1) The project successfully achieved the desired LED chasing effect, where the LEDs light up in a sequential pattern. This visually appealing effect captured attention and demonstrated the versatility of the circuit design.
- 2) The adjustment of the POT-HG potentiometer enabled control over the clock frequency, resulting in varying speeds of the LED chasing effect. It was observed that increasing the clock frequency sped up the sequence, while decreasing the frequency slowed it down, allowing for customization and versatility.
- 3) The project presented opportunities for troubleshooting and error rectification. When issues arose, such as incorrect sequencing or non-

functional LEDs, the process of identifying and resolving these problems improved problem-solving skills and troubleshooting abilities.

- 4) The LED Chaser project served as an educational tool for individuals interested in digital logic design. It provided a practical application of theoretical concepts, fostering a deeper understanding of circuitry, component integration, and hands-on experimentation.

Recommendations:

Based on the project's outcomes, the following recommendations are proposed:

- 1) Experiment with Different LED Configurations: Explore different LED configurations, such as varying the number of LEDs or arranging them in different patterns. This will allow for more diverse and visually interesting chasing effects, expanding the creative possibilities of the project.
- 2) Explore Advanced Functionality: Once a solid foundation is established with the LED Chaser project, consider incorporating additional features or functionalities. This could include integrating external sensors, incorporating a microcontroller for more complex control, or implementing wireless communication to synchronize multiple LED chaser circuits.
- 3) Expand Circuit Complexity: As knowledge and understanding of digital logic design grow, consider expanding the project to incorporate more complex circuits or logic elements. This could involve cascading multiple 4017 decoders to create more intricate chasing patterns or introducing additional logic gates to manipulate the LED sequencing.
- 4) Design an Enclosure or Display: Consider designing and constructing an enclosure or display for the LED Chaser circuit. This will not only provide a more finished and professional appearance but also protect the components and make the project more presentable for demonstrations or exhibitions.

- 5) Collaborate and Share: Engage in collaborative discussions or forums with other electronics enthusiasts or students interested in digital logic design. Share your experiences, findings, and modifications made to the LED Chaser project, and learn from others' projects to further expand your knowledge and creativity in the field.
- 6) Explore Energy Efficiency: Investigate methods to optimize the LED Chaser circuit for energy efficiency. This could involve implementing power-saving techniques, such as using efficient voltage regulators or incorporating a sleep mode to conserve energy when the circuit is not in use.
- 7) Document and Share Modifications: Continuously document any modifications or improvements made to the LED Chaser project. Update the project documentation, circuit diagrams, and component lists to ensure accurate and comprehensive information is available for future reference or when sharing the project with others.

Conclusion:

In conclusion, the LED Chaser project successfully achieved its objectives of demonstrating digital logic design principles and creating an engaging LED chasing effect. By utilizing components such as the 4017 decoder, NE555 timer, capacitors, resistors, and LEDs, the project showcased the integration and functionality of these elements in a practical circuit.

Through the project, individuals gained hands-on experience in circuit design, component integration, troubleshooting, and customization. The adjustable clock frequency provided by the POT-HG potentiometer allowed for versatility and creativity in generating different LED chasing speeds and visual patterns.